

# Half bridge inverter circuit diagram

Half bridge inverter circuit diagram

Submitted by Qamaruddin Khan on Sun, 11/22/2020 - 11:23

Semicon Media is a unique collection of online media, focused purely on the Electronics Community across the globe. With a perfectly blended team of Engineers and Journalists, we demystify electronics and its related technologies by providing high value content to our readers.

The above Fig. 1 shows half bridge inverter using two transistors (MOSFET or IGBT). The diodes are used to protect the IGBT from blocking negative voltage. The diodes allow free-wheeling operation in case of inductive load. When only two switching devices are used for converting DC to AC then the configuration is known as half bridge inverter.

The transistor (MOSFET or IGBT) Q1 is turned ON for a time  $T_o/2$  which makes the  $V/2$  voltage appear across the load, resistance  $R$ . The value of output voltage ( $V_o$ ) is given by

Similarly, when transistor Q2 is turned ON at the instant  $T_o/2$  until time  $T_o$ , by turning OFF Q1 then  $V/2$  voltage appears across the load Resistance  $R$ . The waveforms are shown in Fig. 2. The amount of current flowing through the load is given by,

Contact us for free full report

Web: <https://www.sumthingtasty.co.za/contact-us/>

Email: [energystorage2000@gmail.com](mailto:energystorage2000@gmail.com)

WhatsApp: 8613816583346

## Half bridge inverter circuit diagram

