## **Power inverter circuits**



Power inverter circuits

Power inverters are typically used to create a mains power backup from a set of 12V batteries in the event of a power outage. They are also used in systems where the mains power is supplied by solar panels or wind generators. Power inverters are also an important part of un-interrupted power supplies.

It's important to calculate the current that can be supplied by a power inverter. Otherwise the power inverter might not be able to supply enough current to power your devices. To do this, find the power inverter's VA rating and voltage rating. As an example, if the power inverter's output were rated at 100VA and 110V, the output current would be 100VA / 110V = 0.9A.

A WORD OF CAUTION: This project will involve working with high voltages. This project should only be built if you are trained to work with high voltage electronics. Failure to do so could result in fire, injury, or even death.

The 50Hz oscillator is provided by the 555 timer. Transistor Q1 is an inverting transistor to give a 180? phase shift. The frequency is controlled by potentiometer R5. It can be set to 50Hz or 60Hz.

The drains of the MOSFET transistors are connected to the +12V and -12V sides of mains transformer T1. Since T1 is an inductive load, we need to have two flyback diodes (D1 and D2) to prevent a back EMF spikes from killing the MOSFET transistors.

The size of the mains transformer and the amount of current that can be drawn from the battery will govern how much AC power is available. But in general, if you have a 100VA, 110V transformer, then you should be able to get close to 100VA / 110V = 0.9A. It's only close because the transformer's efficiency will probably be around 70%, so in reality the output current will be closer to about 0.63A.

To analyze the circuit in more detail, I connected the gates of the MOSFETs to an oscilloscope to compare the waveforms at the output and input of the MOSFET circuit. Note that they are 180? out of phase:

Hi,I would like to know if we change the "555" part with a sinusoidal generator, the inverter will also work? Will it deliver a sinusoidal 220 Volt output in this case?Many thanks.Lahcene Akrour

the mosfet need a sharp wave, full open or full closed tween this, the mosfet is 'only' a resistor and heats up – this 'time in the middle' must reduced to a minimum.

if you want sinusoidal, you must generate variable output voltage with a higher frequence, so you can between the steps higher the voltage to rise, lower then to fall to zero, lower to fall to -12, rice to zero, rise to +12 and so on.



## **Power inverter circuits**

Thanks for explaining power inverters. A power inverter is a tool to convert DC power to AC power. We need AC power to run all those devices that require AC power. However, there are many DC devices that can be connected with a 12V battery, in this case, you may not need a power inverter.

Contact us for free full report

Web: https://www.sumthingtasty.co.za/contact-us/ Email: energystorage2000@gmail.com WhatsApp: 8613816583346

